

SleepyU CPU Manual

Yash Parmar & Nikunj Patel

Professor Hao
CS382-B

11 December 2025

Contents

1 CPU Name and Contributors	3
1.1 Contributions	3
2 Setup Instructions	3
3 Architecture Description	4
3.1 CPU Components	4
3.1.1 Instruction Fetching Stage	4
3.1.2 Instruction Decoding Stage	4
3.1.3 Execution Stage	4
3.1.4 Memory Access Stage	4
3.1.5 Write Back Stgae	4
3.1.6 Register File	5
4 Naming Conventions	5
5 Instruction Format (8-bit)	5
5.1 Instruction Encodings	5

1 CPU Name and Contributors

Name: SleepyU

Contributors: Yash Parmar & Nikunj Patel

1.1 Contributions

Yash Parmar:

- Designed and organized the stages in the datapath.
- Developed the assembler program with help from Nikunj on opcode encodings.
- Assisted in writing the manual.

Nikunj Patel:

- Defined control signals and opcode encodings with help from Yash on datapath design.
- Developed the demo program for the CPU.
- Assisted in writing the manual.

2 Setup Instructions

1. Run the startup command to assemble the demo program:

```
1 bash startup.sh
```

1. Load `demo_instruction.hex` into Instruction RAM.
2. Load `demo_memory.hex` into Data RAM.
3. Press **Simulate** and then **Timing Diagram**.
4. Press **Manual Tick Half Cycle** to half tick into the first cycle.
5. Set initial register values in Register File:
 - X0: 00
 - X1: 00
 - X2: 01
 - X3: 00
6. Run the simulation for 6 clock cycles (Press **Manual Tick Full Cycle** 6 times).
7. The first value in Data RAM should be 43 or 0x43 (or 67 in decimal).

3 Architecture Description

- 4 general purpose registers: X0, X1, X2, X3.
- Supported instructions: BOOST (ADD), FALL (SUB), FETCH (LDR), TUCK (STR).
- PC register increments by 1 after executing each instruction.
- Single-clock-cycle design: all instruction steps (fetch, decode, execute, memory access, write-back) happen in one cycle.

3.1 CPU Components

3.1.1 Instruction Fetching Stage

- Fetch instruction from Instruction RAM using PC.

3.1.2 Instruction Decoding Stage

- Decode opcode and determine registers and control signals:
 - WriteEnable: 1 if BOOST, FALL, FETCH; 0 for TUCK
 - ALUOp: 1 for FALL; 0 for BOOST, FETCH, TUCK
 - MemRead: 1 for FETCH; 0 otherwise
 - MemWrite: 1 for TUCK; 0 otherwise
 - MemToReg: 1 for FETCH; 0 otherwise

a

3.1.3 Execution Stage

- Perform addition (BOOST, FETCH, TUCK) or subtraction (FALL) as determined by ALUOp.

3.1.4 Memory Access Stage

- Use ALU output as address or computation depending on instruction.
- Load or store data depending on MemRead/MemWrite signals.

3.1.5 Write Back Stgae

- Write either ALU output or memory data to the destination register based on MemToReg.

3.1.6 Register File

- Read source registers and destination register using 2-bit addresses.
- Output 8-bit register values.

4 Naming Conventions

- BOOST: ADD
- FALL: SUB
- FETCH: LDR
- TUCK: STR
- Rd: destination register
- Rs: source register
- Rt: target register
- Rm: operand register 1
- Rn: operand register 2

5 Instruction Format (8-bit)

- [aa bb cc dd]:
 - 2-bit opcode (aa): identifies instruction (BOOST, FALL, FETCH, TUCK)
 - 2-bit destination register (bb): X0-X3
 - 2-bit source/operand register (cc): X0-X3
 - 2-bit target/operand register (dd): X0-X3
- Reasoning: 8-bit instruction allows minimal memory usage and easy scalability.

5.1 Instruction Encodings

- BOOST (BOOST Rd, Rm, Rn): opcode = 00
- FALL (FALL Rd, Rm, Rn): opcode = 01
- FETCH (FETCH Rd, [Rs, Rt]): opcode = 10
- TUCK (TUCK Rd, [Rs, Rt]): opcode = 11

Hope you enjoy our SleepyU!